README.md 10/18/2021

Vypracovanie LAB_3 - Alexander Bekeč

Alexander Bekeč, 221096

Link to depository: https://github.com/alexander-bekec/Digital-electronics-2

Overflow times

1. Complete table with overflow times.

Module	Number of bits	1	8	32	64	128	256	1024
Timer/Counter0	8	16us	128us		1.024 ms		4.096 ms	16.384 ms
Timer/Counter1	16	4.096 ms	32.786 ms		262.144 ms		1.049 s	4.194 s
Timer/Counter2	8	16us	128us	512 us	1.024 ms	2.048 ms	4.096 ms	16.384 ms


Timer library

- 1. In your words, describe the difference between common C function and interrupt service routine.
 - Function časť programu, ktorá beží nonstop, permanentne kontroluje stavy, plne spotrebúva spracovací čas procesoru
 - Interrupt service routine časť programu, ktorá sa vykoná len v prípade prerušenia, resp. zmeny stavu, a po vykonaní nespotrebúva spracovací čas procesoru
- 2. Part of the header file listing with syntax highlighting, which defines settings for Timer/Counter0:

```
/**
 * @name Definitions for 8-bit Timer/Counter0
 * @note t OVF = 1/F CPU * prescaler * 2^n where n = 8, F CPU = 16 MHz
/** @brief Stop timer, prescaler 000 --> STOP */
#define TIM0 stop()
                             TCCR0B &= ~((1<<CS02) | (1<<CS01) | (1<<CS00));
/** @brief Set overflow 16us, prescaler 001 --> 1 */
#define TIM0_overflow_16us() TCCR0B &= \sim((1<<CS02) | (1<<CS01)); TCCR0B |=
(1<<CS00);
/** @brief Set overflow 128us, prescaler 010 --> 8 */
#define TIM0 overflow 128us() TCCR0B \&= \sim((1<<CS02) \mid (1<<CS00)); TCCR0B \mid=
(1<<CS01);
/** @brief Set overflow 1ms, prescaler 011 --> 64 */
#define TIM0_overflow_1ms() TCCR0B &= ~(1<<CS02); TCCR0B |= (1<<CS01) | (1<<CS00);
/** @brief Set overflow 4ms, prescaler 100 --> 256 */
#define TIM0_overflow_4ms() TCCR0B &= \sim((1<<CS01) | (1<<CS00)); TCCR0B |=
(1<<CS02);
```

README.md 10/18/2021

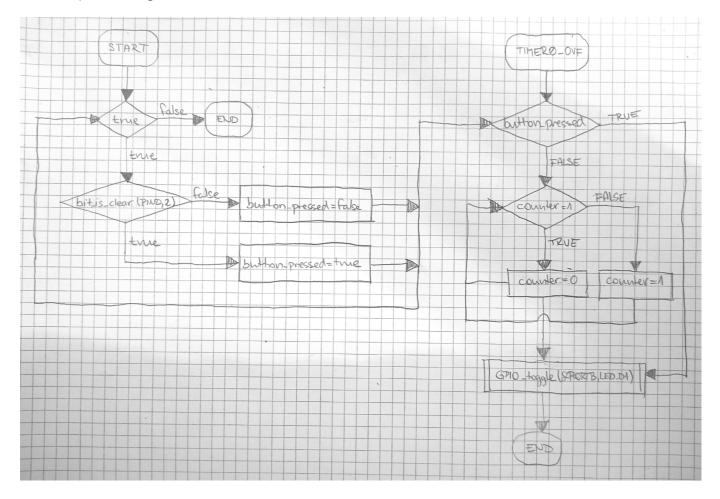3. Flowchart figure for function main() and interrupt service routine ISR(TIMER1_OVF_vect) of application that ensures the flashing of one LED in the timer interruption. When the button is pressed, the blinking is faster, when the button is released, it is slower. Use only a timer overflow and not a delay library. The image can be drawn on a computer or by hand. Use clear descriptions of the individual steps of the algorithms.



Knight Rider

1. Scheme of Knight Rider application with four LEDs and a push button, connected according to Multifunction shield. Connect AVR device, LEDs, resistors, push button, and supply voltage. The image can be drawn on a computer or by hand. Always name all components and their values. README.md 10/18/2021

